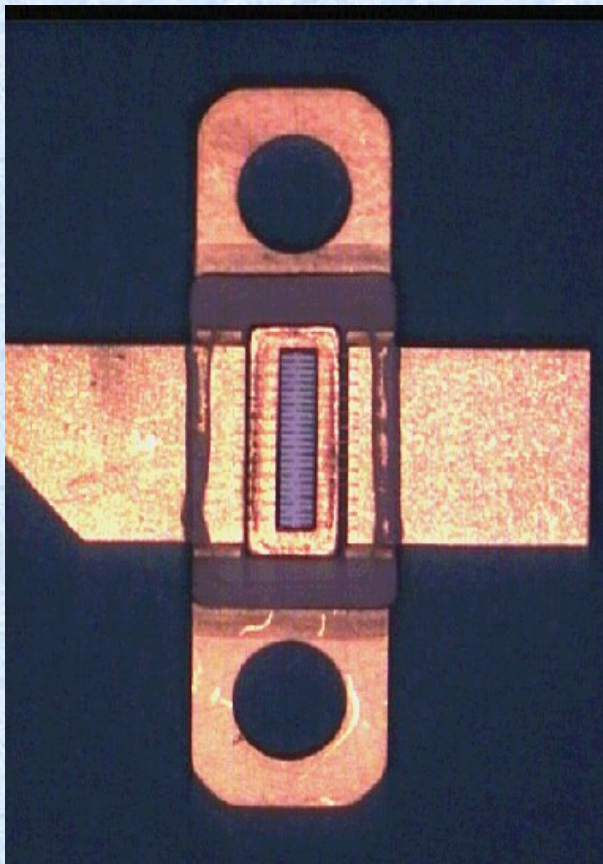


The Bodger's Guide to Solid State QRO at VHF



or

How to get serious VHF power without potential electrocution!

John Worsnop G4BAO



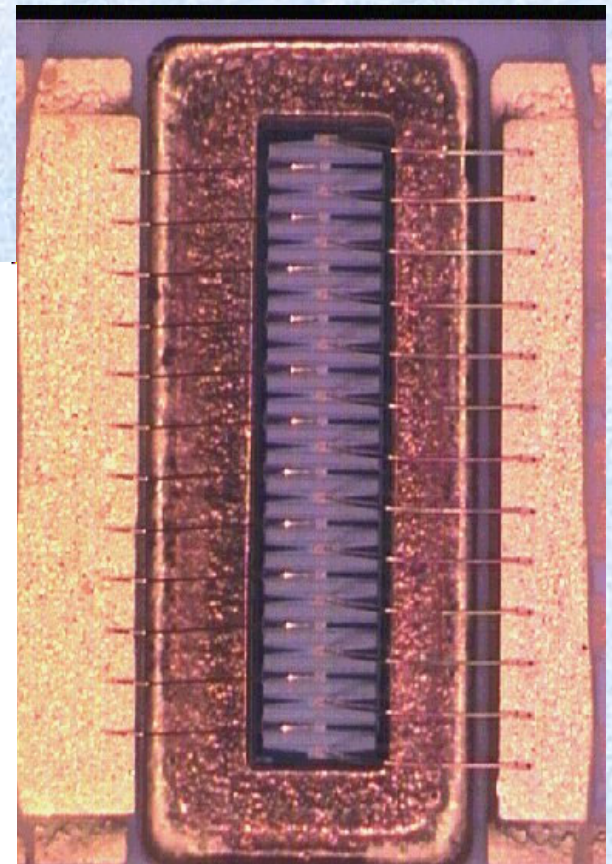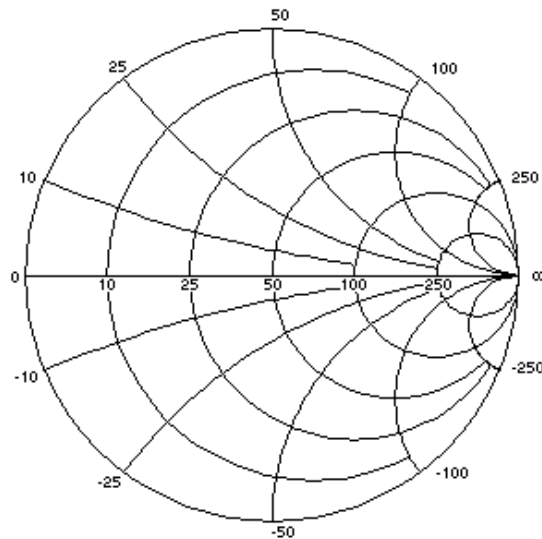Laterally **D**iffused **M**etal
Oxide **S**emiconductor



© Bravo Alpha Oscar 2010


The Bodger's Guide to Solid State QRO at VHF

John Worsnop G4BAO

- Bodger – (noun)
 - A highly skilled itinerant wood-turner, who worked in the beech woods on the chalk hills of the Chilterns, in England
- Bodging (Br. Slang)
 - an inexpertly or roughly done job, typically in the field of DIY.




- Modified N-channel MOSFET.
- Three terminals of the transistor are accessible from the top of the chip.
- and source is at the bottom allowing direct connection to ground.
- No nasty beryllium oxide insulator needed.
- matching circuitry can be added within the transistor package.
- Devices that operate up to about 4GHz
- Vdd typically 28 or 50V.
- 800 Watt plus devices at VHF
- Simple positive gate bias circuitry.
- Hard to destroy in development.

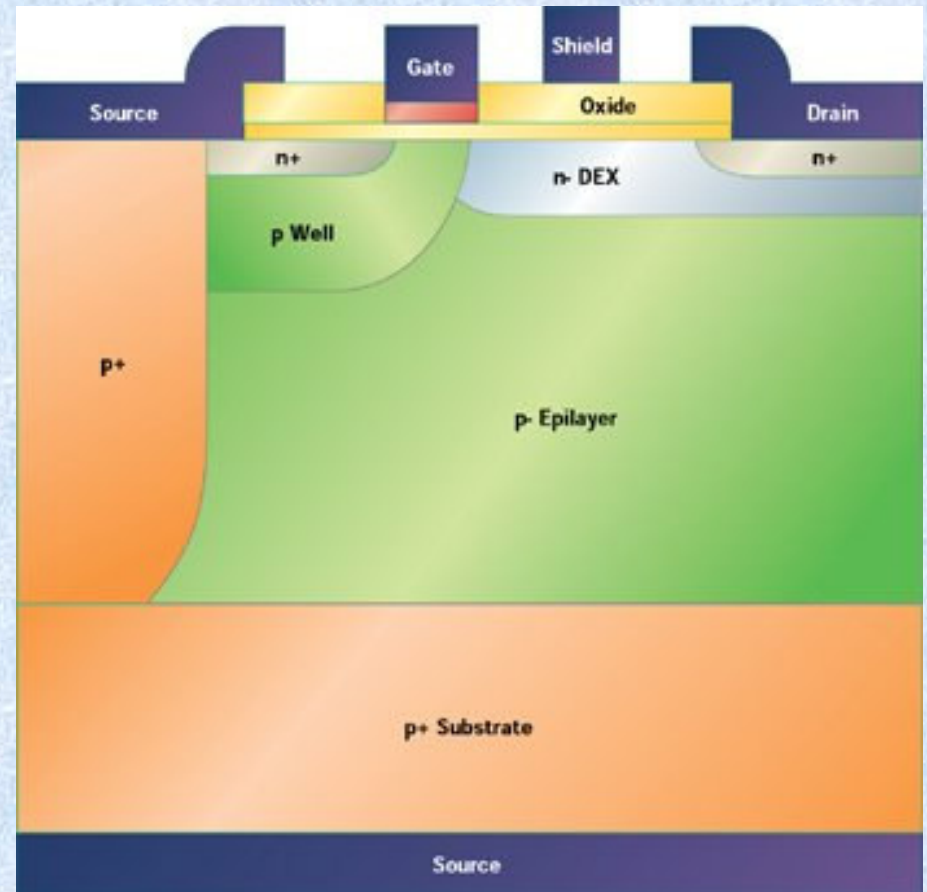




Devices- The previous generation

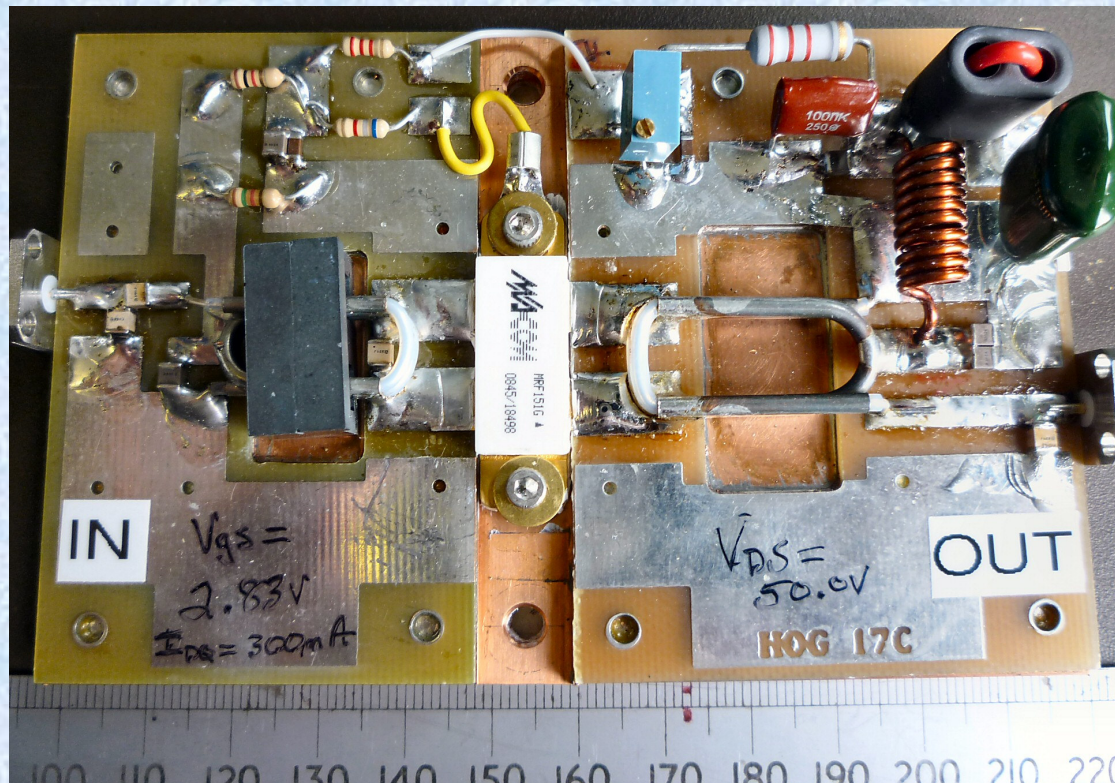- The legendary MRF151G “Gemini” device
 - 300Watts out 15dB Gain to 144MHz VSWR 5:1
 - Some surplus amplifiers available




Devices- What's available now?

- Freescale
 - Single ended
 - MRF6V2300 – 300 Watts 24dB gain 10-600MHz - \$83
 - “Gemini”
 - MRF6VP2600 400 Watts 24dB gain 10-250MHz - \$150
 - VSWR 10:1
 - MRF6VP41kH 800 Watts 22dB gain 10-500MHz - \$610
 - VSWR 10:1 (DL4XX 800W amp for 2m)
 - And coming soon
 - **MRFE6VP6300H** 1.8-600MHz; 300 watt CW
 - rated up to 65:1 VSWR in CW!
 - All these are 50 Volt devices
- Microsemi
 - ARF467FL
 - Rated for pulsed operation to 900Watts Peak!
 - 150 Volt supply

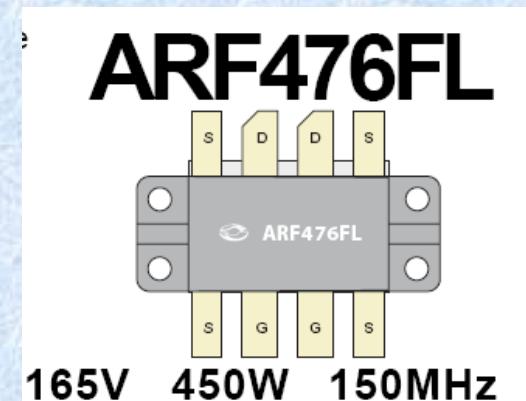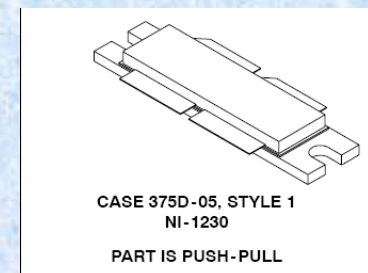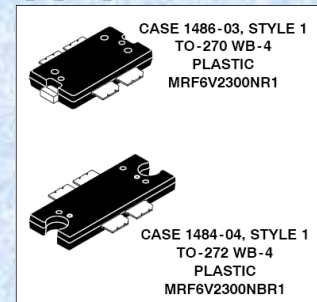

It's the impedances, stupid!

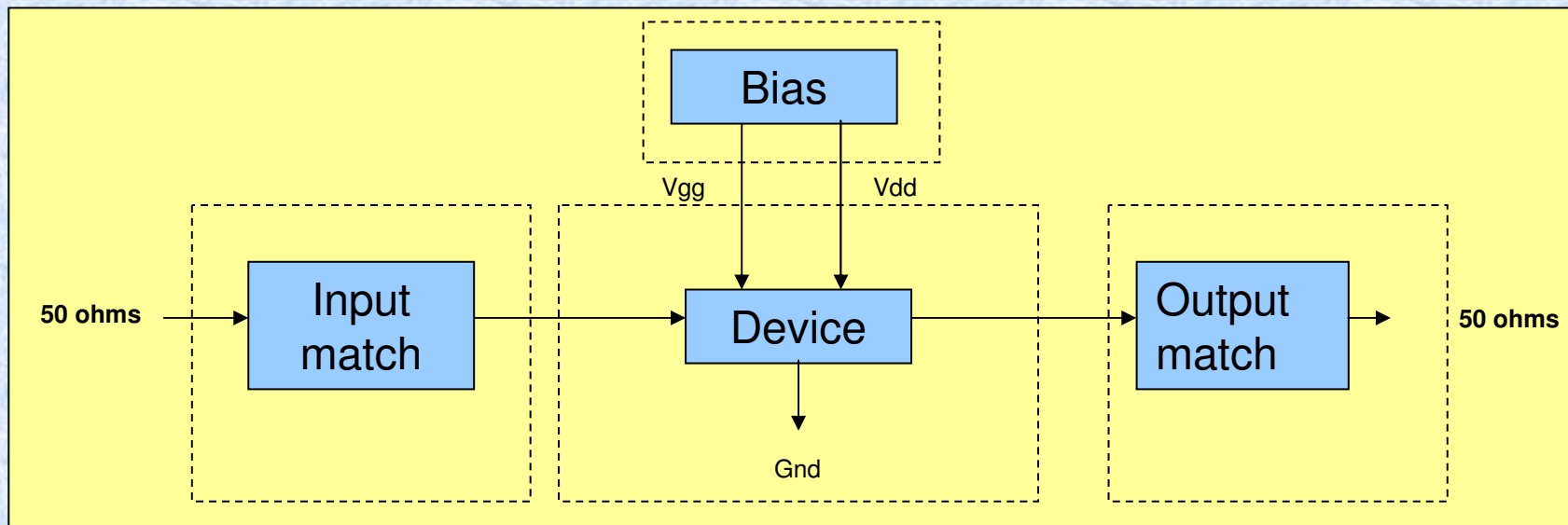- Power transistors are low impedance devices.
- Typically less than 50ohm, resistive and reactive
- You have to match them to 50ohms
- Matching circuits have a bandwidth




It's the impedances, stupid!

- So the (Bodger's) design process is:
 - Make the device input look like 50 ohms by transforming its input impedance over the required bandwidth.
 - Make sure the device "sees" the correct impedance load for the power level
 - Make sure the impedance matching doesn't make the amplifier unstable at other frequencies.

Z_{source} = Test circuit impedance as measured from gate to ground.

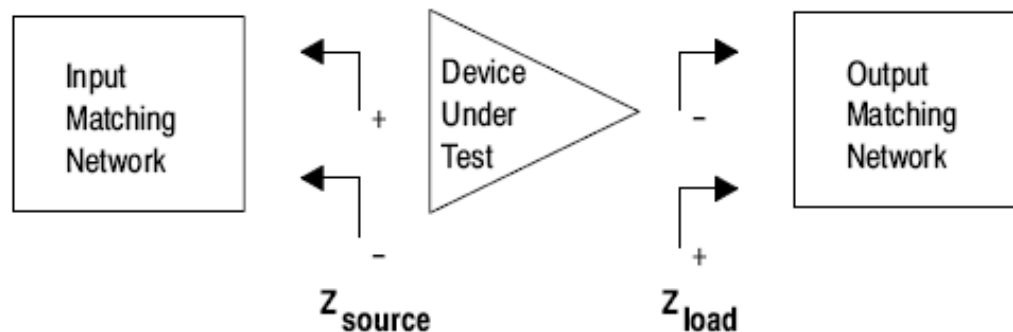Z_{load} = Test circuit impedance as measured from drain to ground.



So we need the device datasheets, right?

- **WRONG!**
 - Fine if data is available for the frequency you need
- Much VHF LDMOS is designed for broadcast
- 88-108MHz, 225MHz, 470-860 MHz


So we're stuck?

- Amateurs don't have the technology to measure device impedances.
- So let's call upon.....

The Bodger's subroutine!


Applicable to a "new" design or retuning surplus
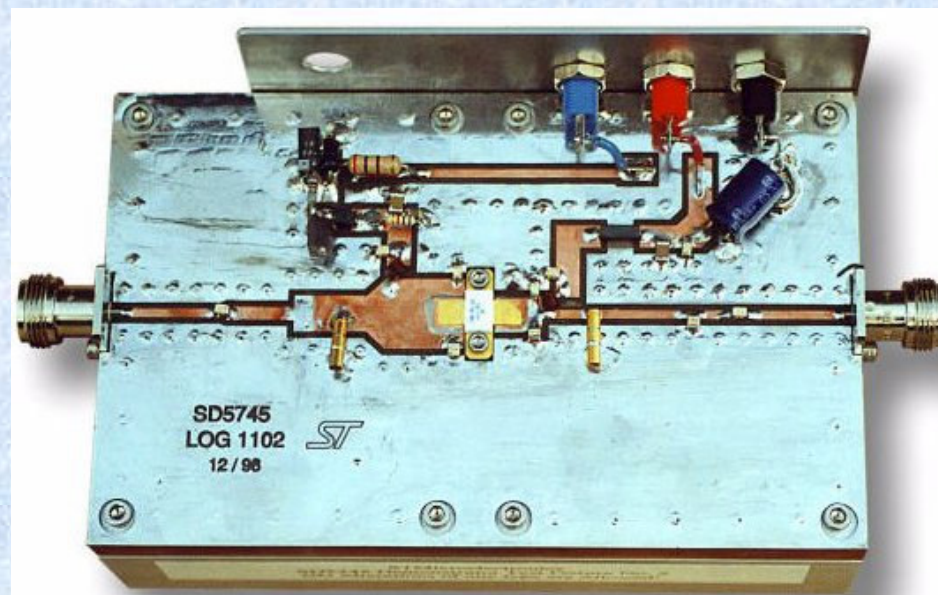
```
make intelligent stab at what  
  you think might work  
then  
  repeat  
    cut  
    try  
    optimise  
  until working satisfactorily  
end
```




Output matching for Bodgers

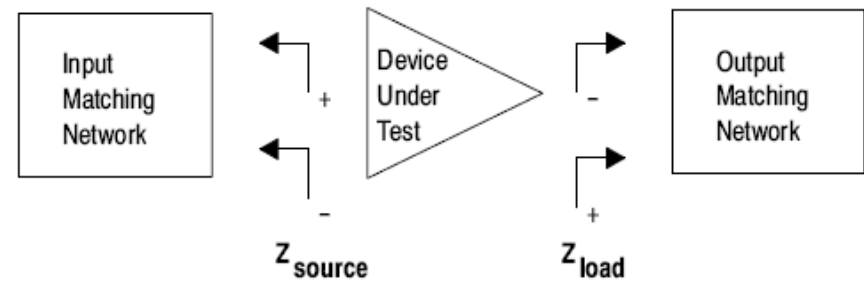- Drain voltage swings from V_{dd} to $V_{dd_{on}}$
- This is approximately 0 to V_{dd}
- If we assume the waveform is sinusoidal




Equivalent circuit for LDMOS

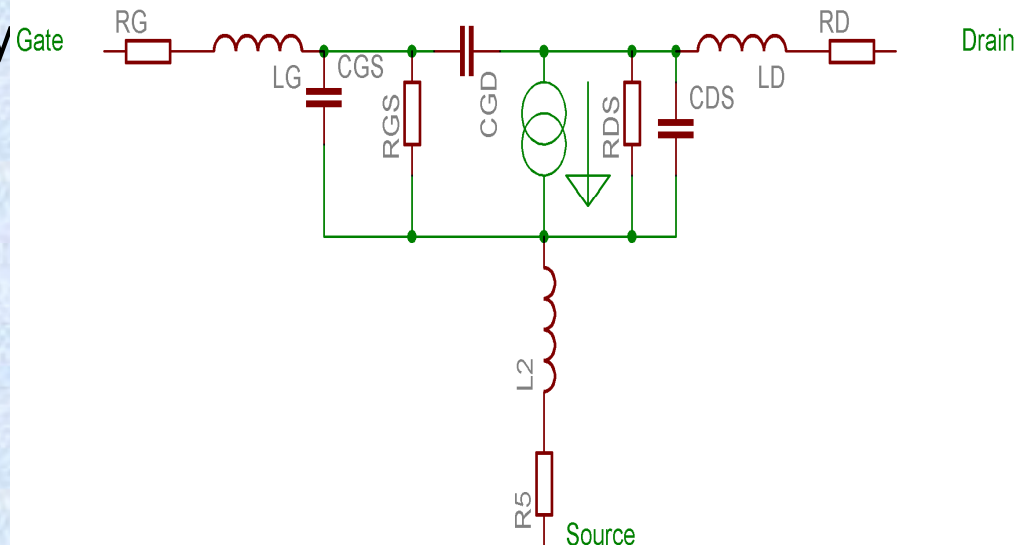- Output power is approximately
- $P_{out} = V_{dd}^2 / 2R_{Load}$




Output matching for Bodgers

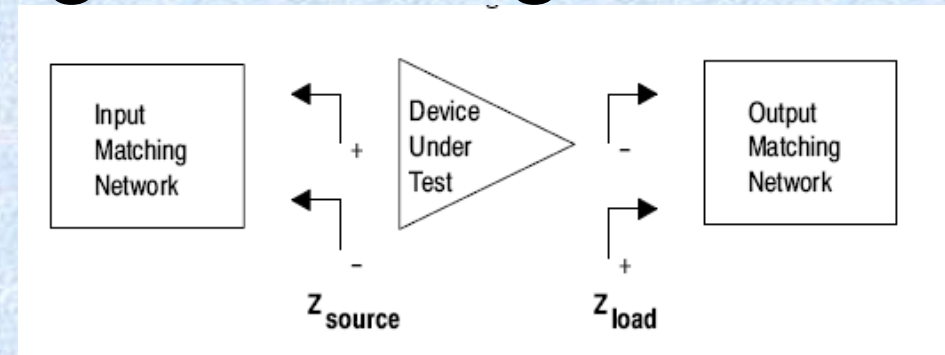- So to deliver the power, the device needs to “see”
- $R_{Load} = V_{dd}^2 / 2P_{out}$
- We have C_{DS} in parallel with the device
- So our network must resonate this out as well (conjugate matching)



Equivalent circuit for LDMOS

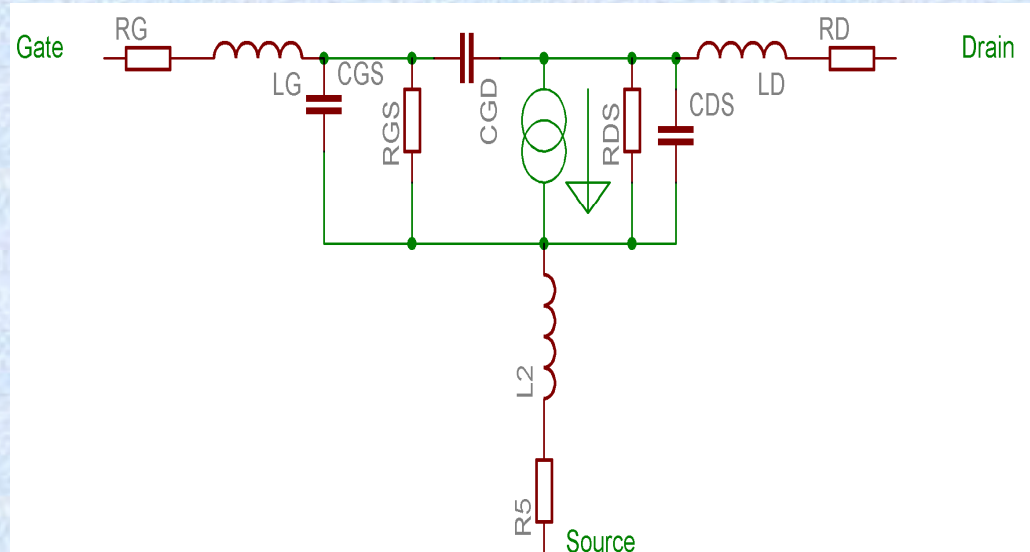

Output matching for Bodgers


- So we have our output network requirements!
- $R_{\text{Load}} = V_{\text{dd}}^2 / 2P_{\text{out}}$
- in parallel with conjugate of C_{DS}
- But I prefer series circuits because impedances add.
- So
- Convert this to a series $R + jX$ format using Maths or a Smith Chart.

Example 6VP2300H device at $P_{out} = 300\text{Watts}$, 50 Volts

- This gives $R_{Load} = 4.16$ ohms in parallel with $C_{DS} = 120\text{pF}$
- Convert this to a series combination and conjugate it.
 - $Z_L = 3.2 + j1.76$ ohms
- Compare this to the datasheet value of $2.7 + j2.2$ ohms
- Close enough?
- Time to get out the Smith Chart


A brief aside on the Smith Chart

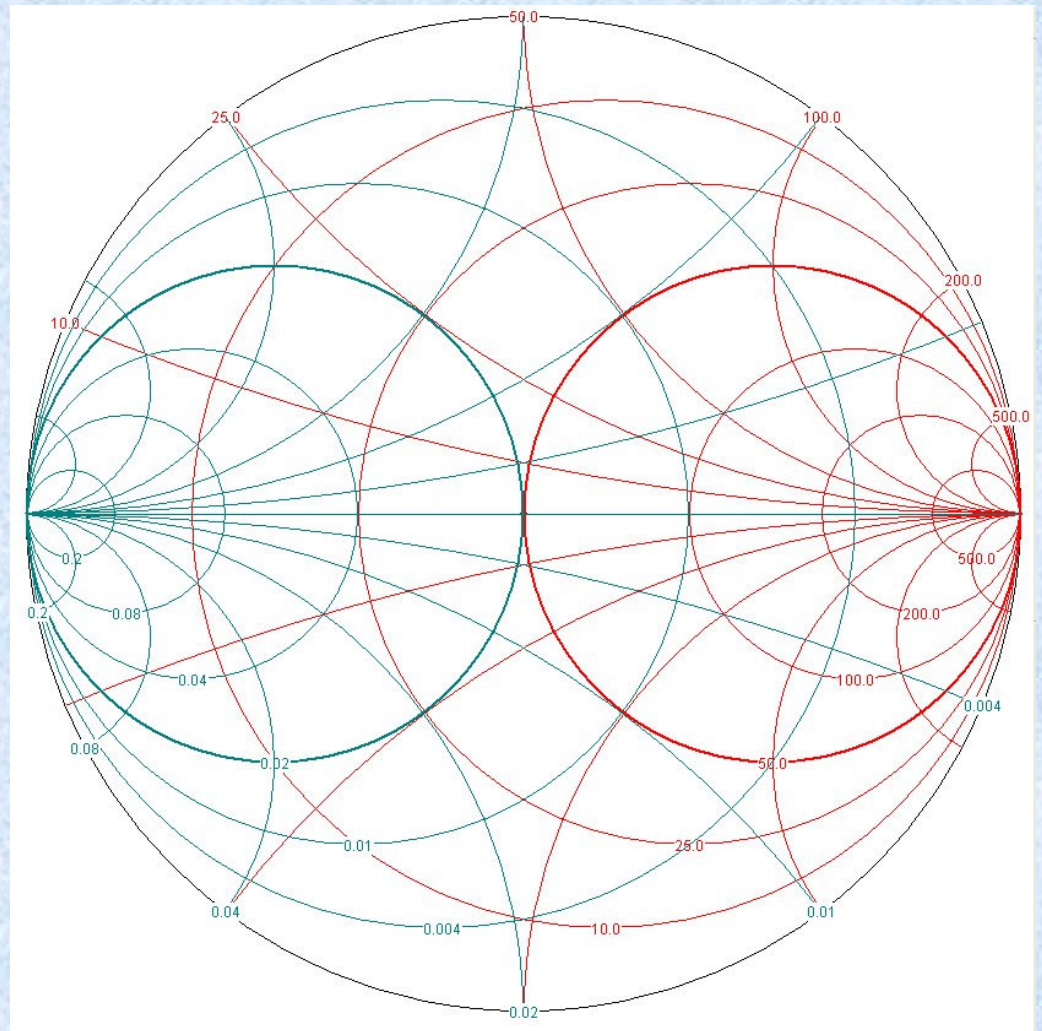- **“Immittance” Chart**
- A whole day could be given over to its usage
- It allows you to plot complex impedances, admittances and line lengths.




A brief aside on the Smith Chart

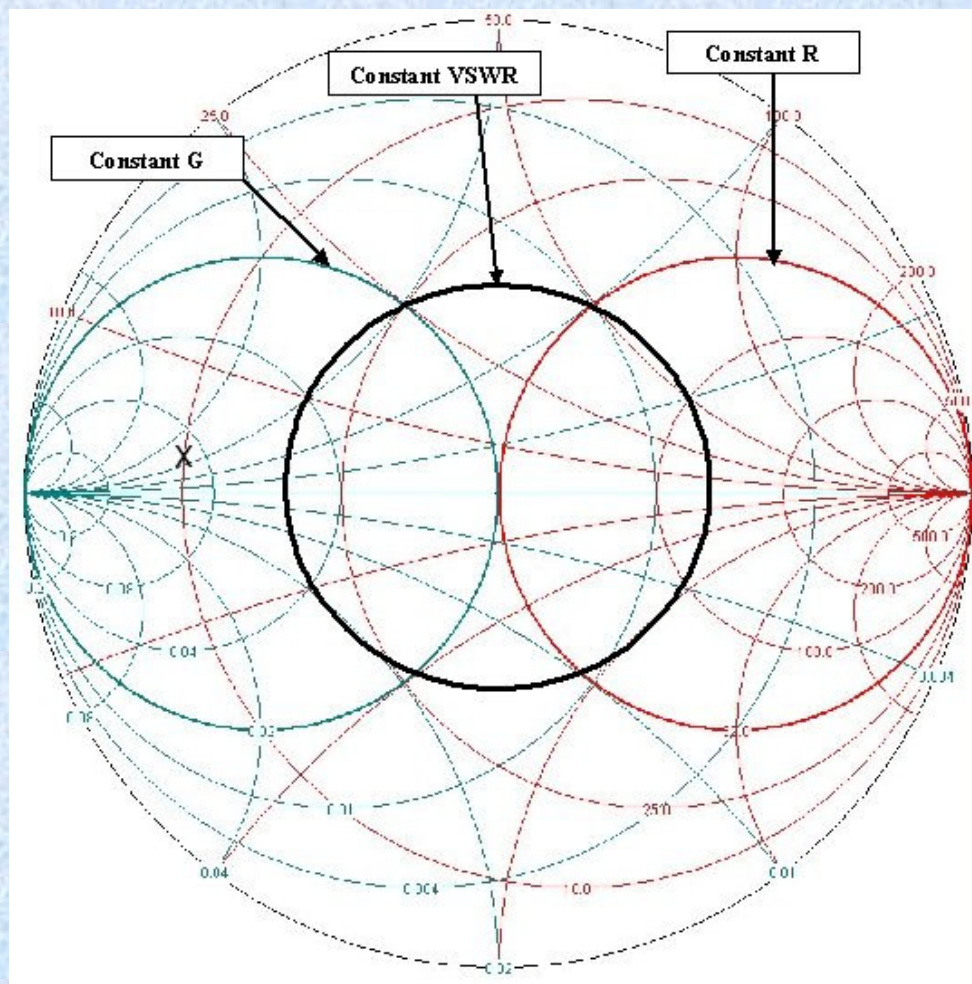- Series L or C moves you along constant R circle
- Shunt C or L moves you along constant G circle.




A brief aside on the Smith Chart

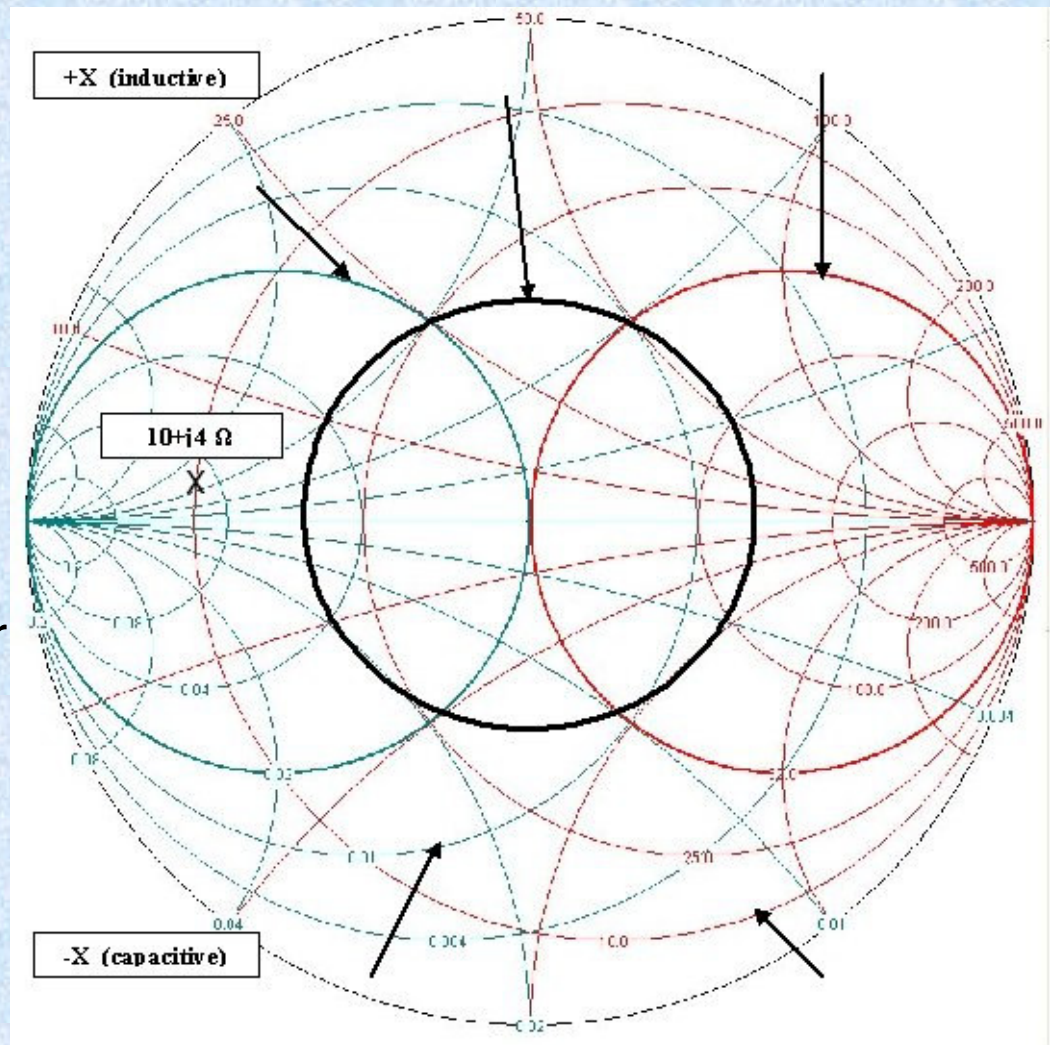- Usually use “normalised” impedances,
 - i.e (actual Z)/ Z_0
- Positive reactances (Inductive) are in the upper half of the chart
- Negative reactances (Capacitive) are in the lower half of the chart
- Impedance can be plotted directly



The Bodger's Guide to Solid State QRO at VHF

John Worsnop G4BAO

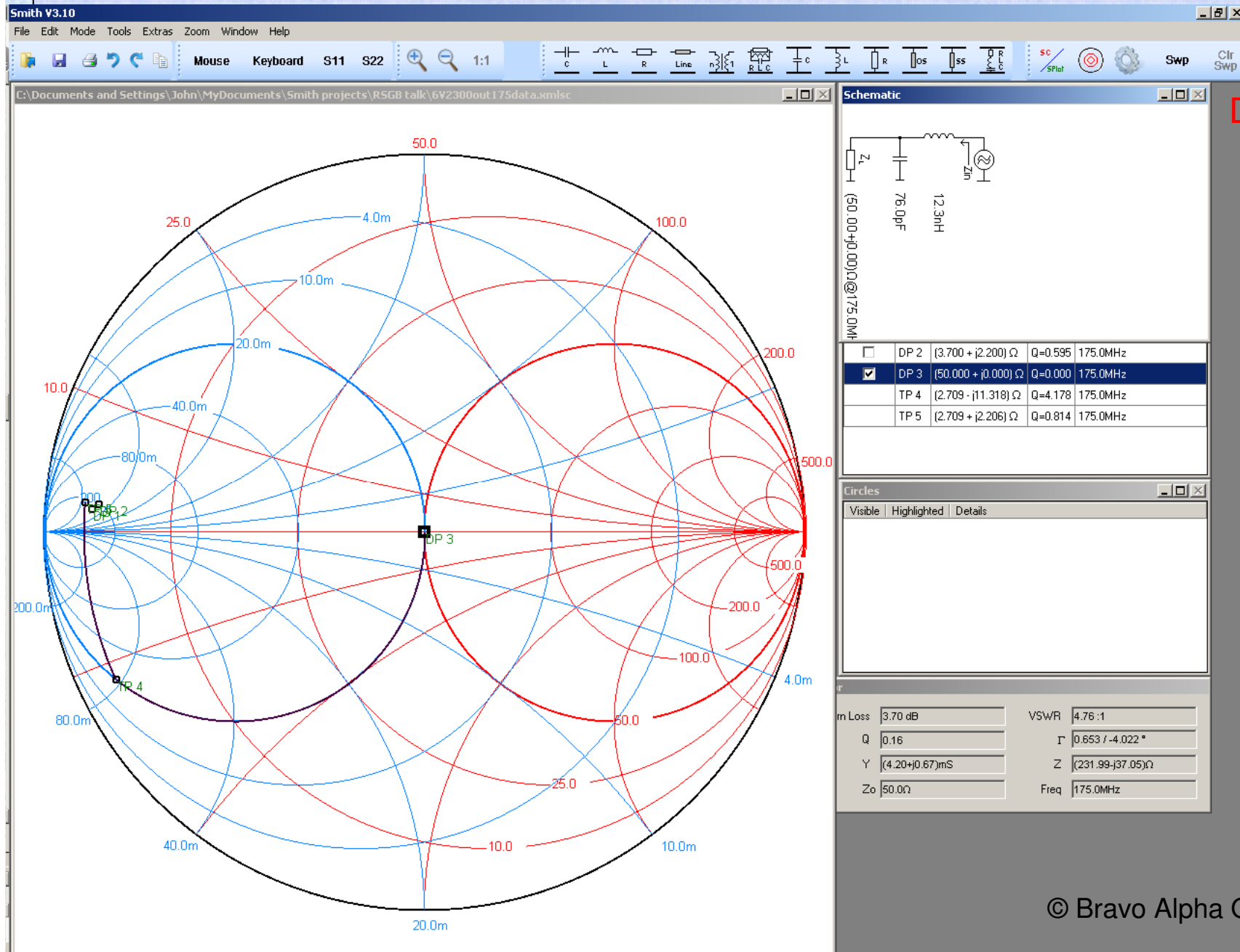


Datasheet

12.3nH
76pF

© Bravo Alpha Oscar 2010

The Bodger's Guide to Solid State QRO at VHF

John Worsnop G4BAO

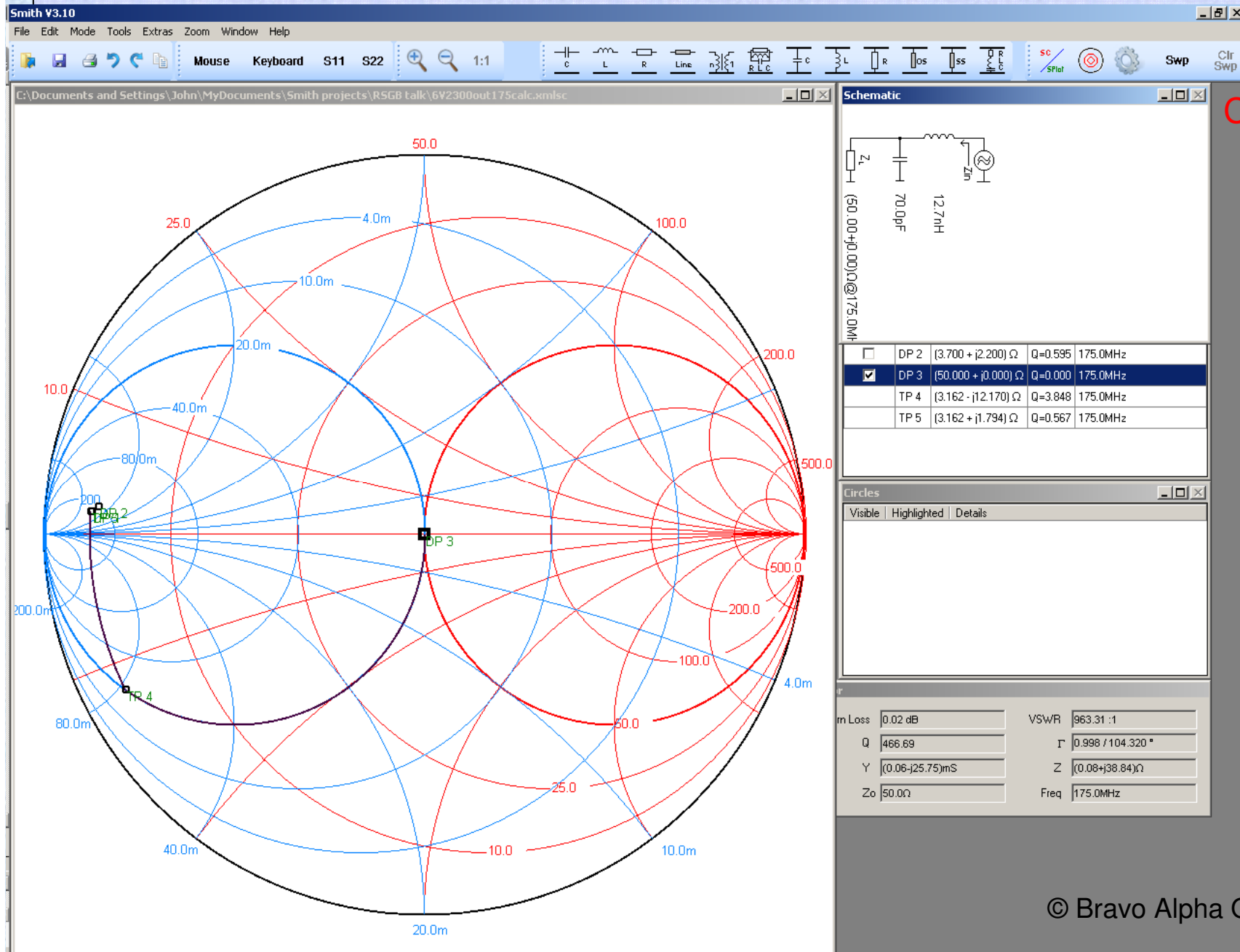


Calculated

12.7nH
70pF

© Bravo Alpha Oscar 2010

The Bodger's Guide to Solid State QRO at VHF

John Worsnop G4BAO

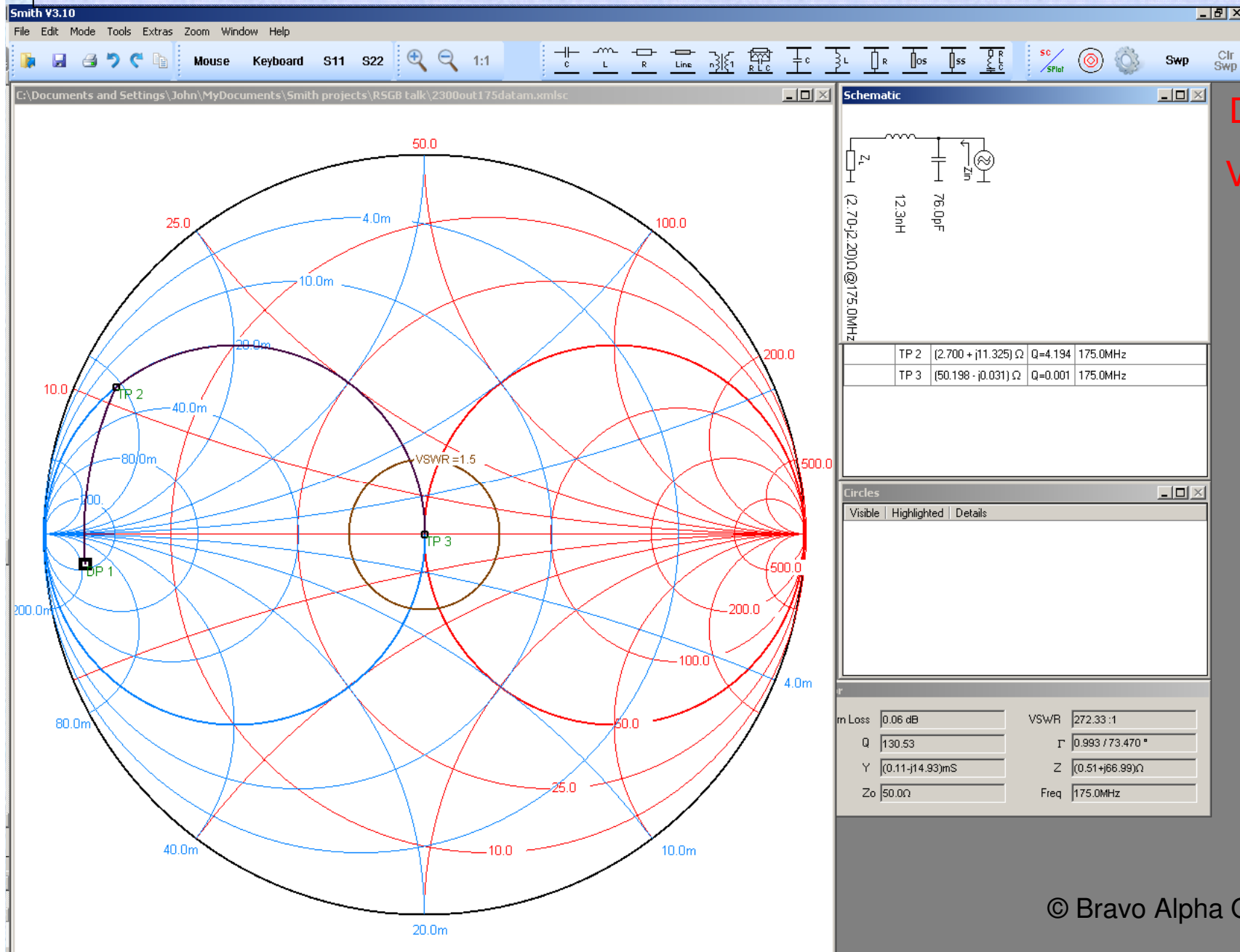


Datasheet
VSWR 1:1

© Bravo Alpha Oscar 2010

The Bodger's Guide to Solid State QRO at VHF

John Worsnop G4BAO

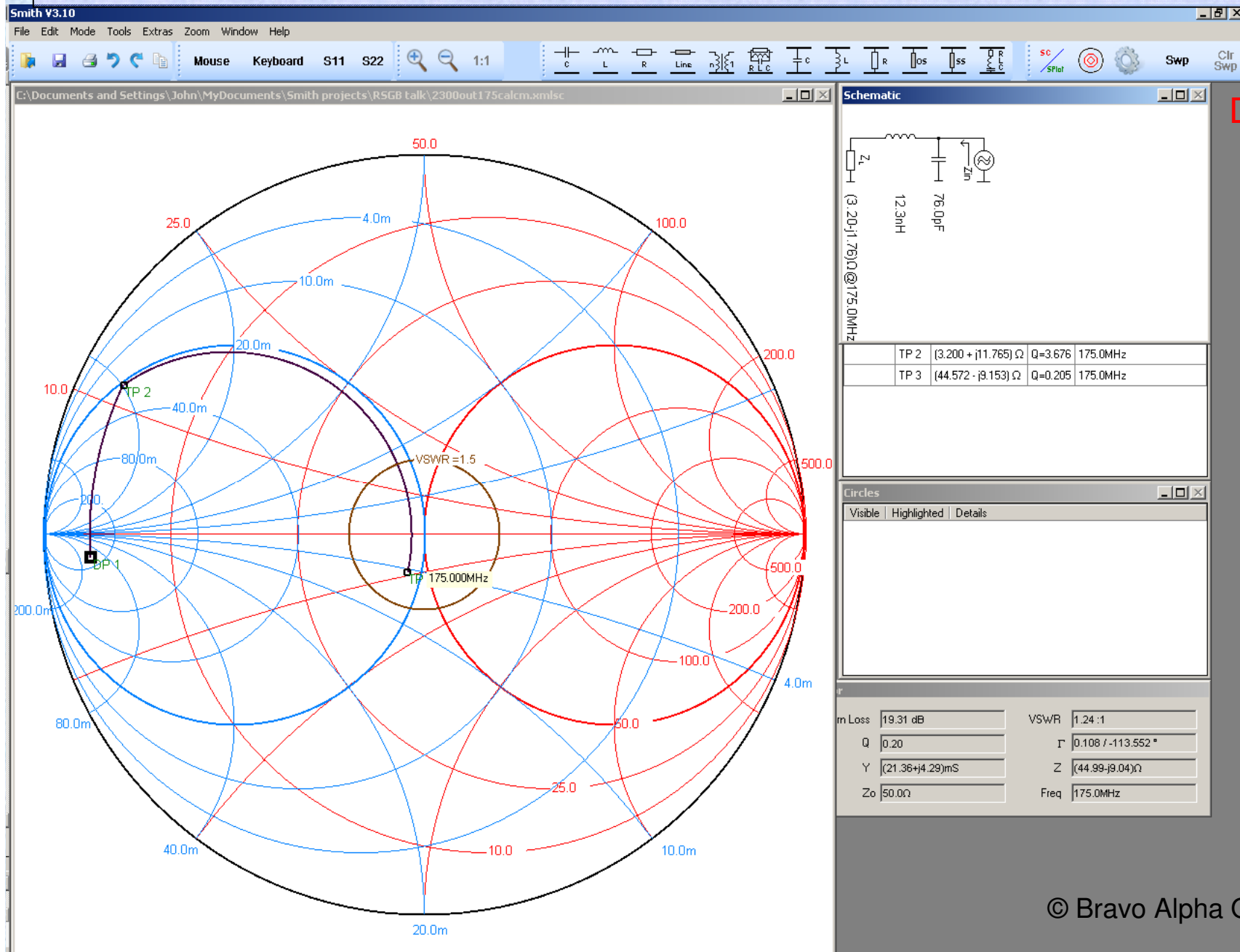


Datasheet

VSWR
1.24:1



© Bravo Alpha Oscar 2010

Gemini Devices - Transformer matching

- Gemini devices are two devices in one package
- Designed for Push-pull operation
- Transformers allow balun and impedance transformation

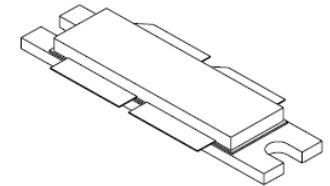


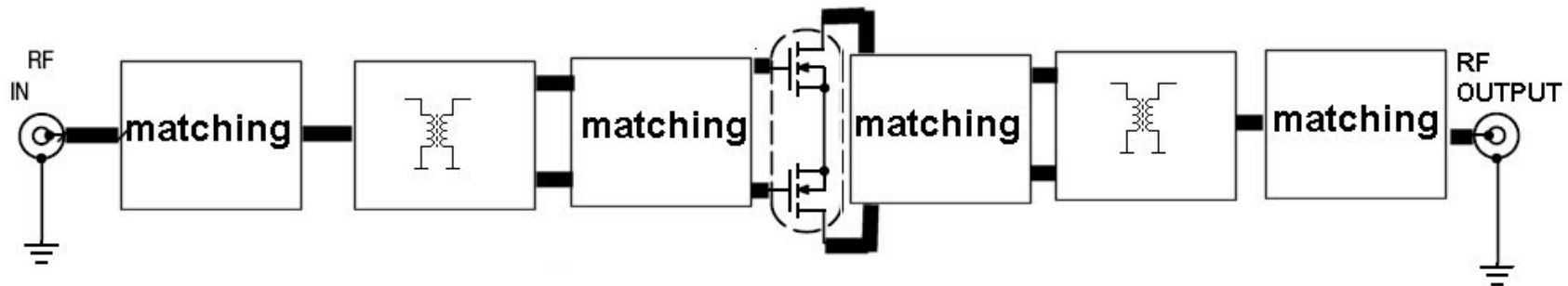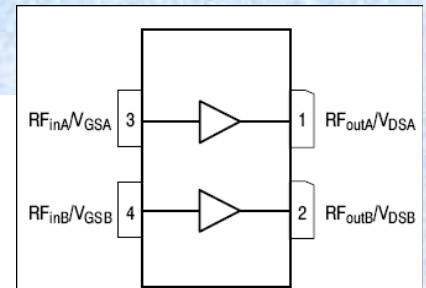CASE 375D-05, STYLE 1
NI-1230
PART IS PUSH-PULL



The Bodger's Guide to Solid State QRO at VHF

John Worsnop G4BAO

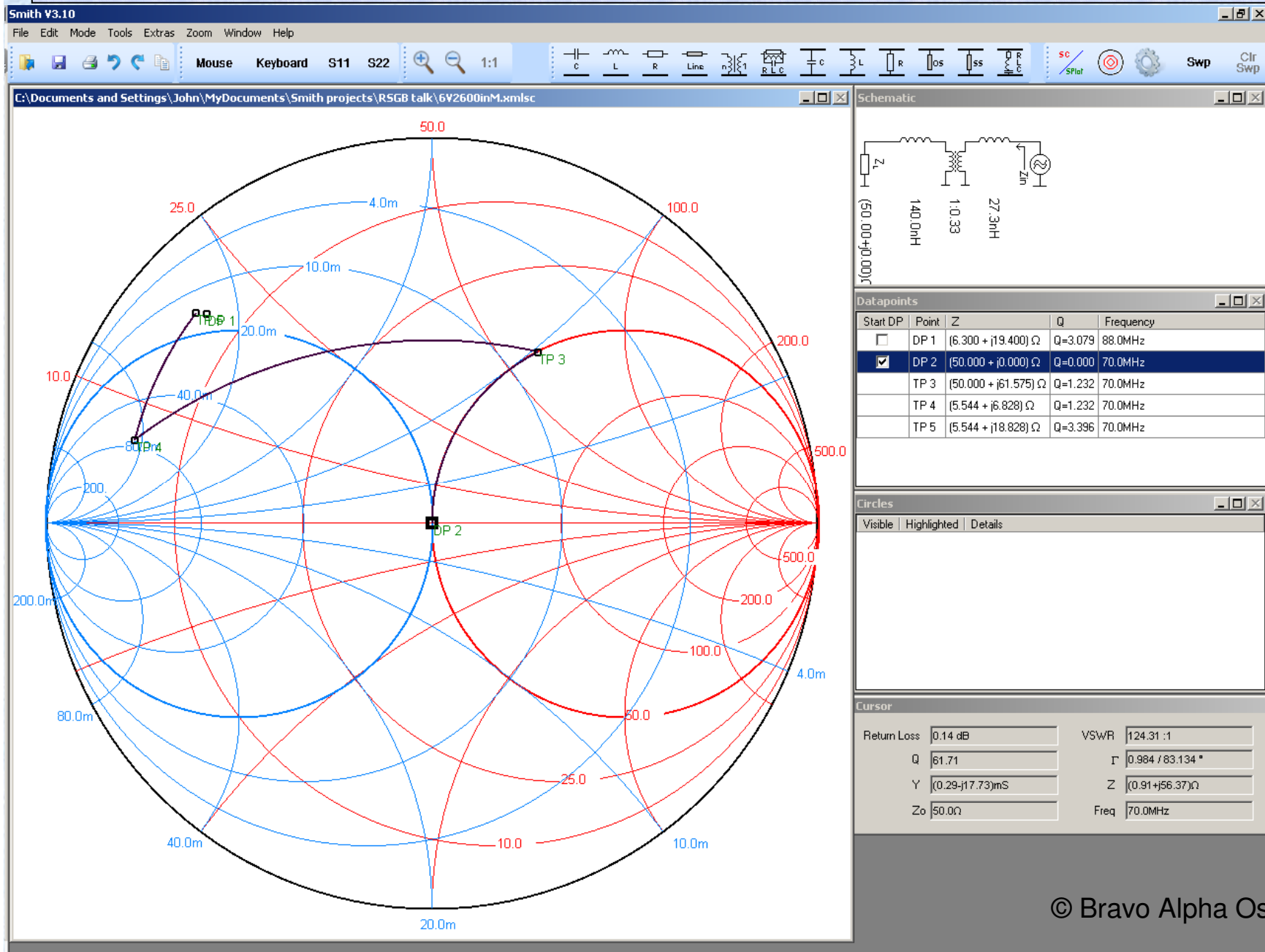


© Bravo Alpha Oscar 2010

Device mounting -The choices


Bolt



Clamp

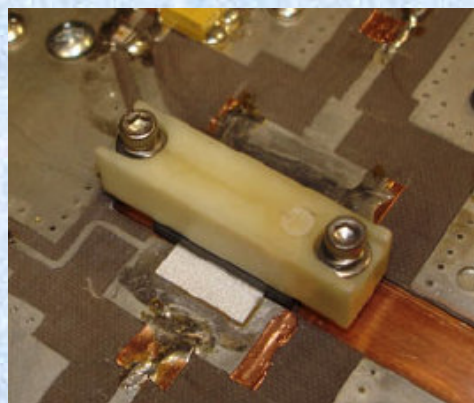

Solder

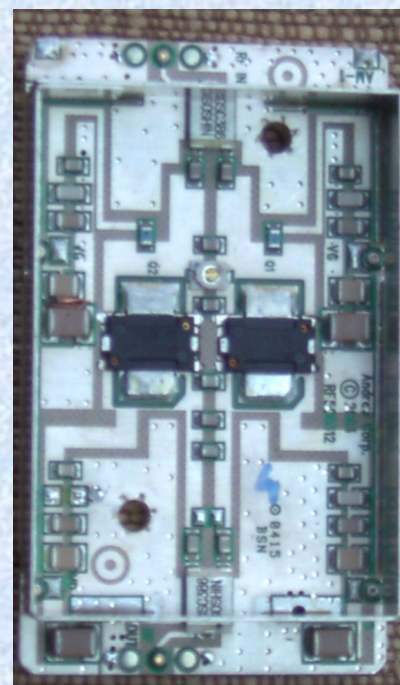

Device mounting - clamping vs bolting


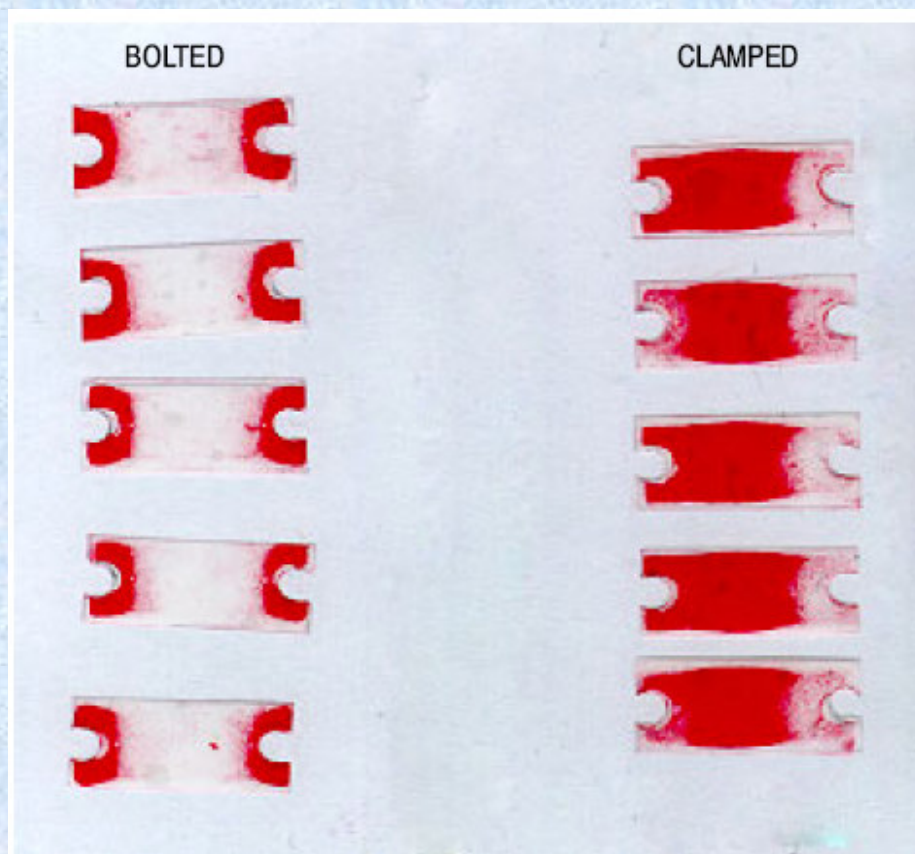


Figure 7. Pressure Paper Test Results for Five TO-272WB Packages with #4-40 Screws at a Mounting Torque of 4.0 in-lb

Source Freescale AN-3789

Device mounting – Typical clamp design

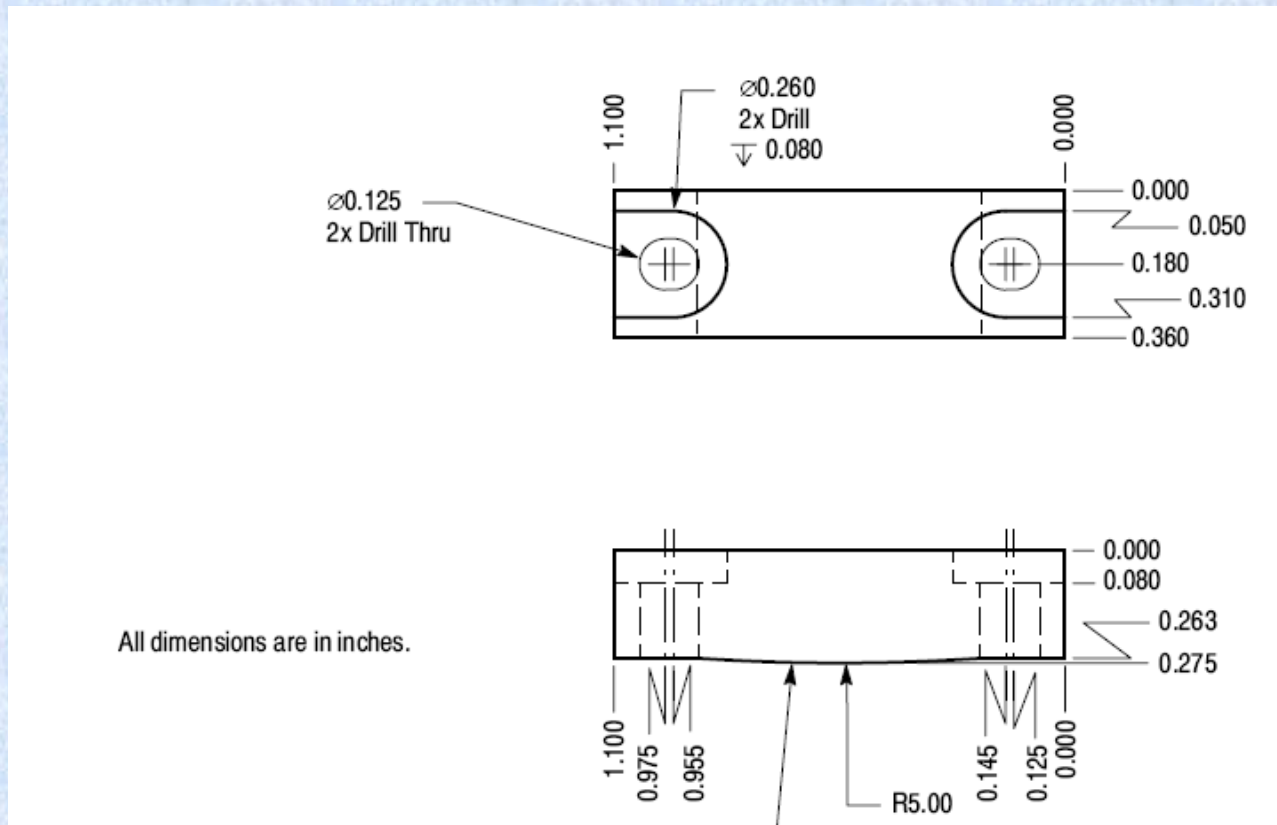


Source Freescale AN-3789

© Bravo Alpha Oscar 2010


Device mounting – Getting the heat away

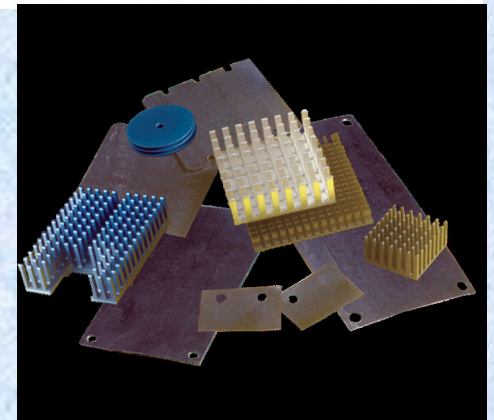- Use a copper heat spreader!!
- Interface material
 - Nothing when clamping, if the copper heat spreader is flat enough
 - Conductive grease (RS)
 - 0.125mm T-GON805 (graphite sheet)
 - (Mouser)





A 144MHz design with the 6V2300

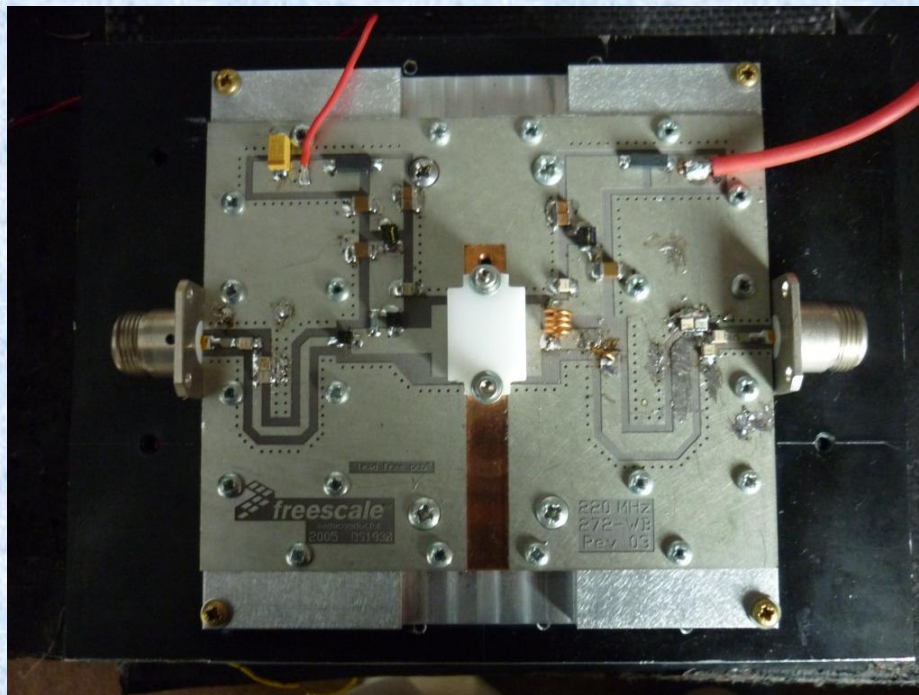- Measured 270 Watts on 2m for 800mW drive.
- Flangeless device clamped down with PTFE clamp.
- Narrow band matching – but no trimmers.
- Currently on Freescale test board.
- Eagle PC design done with bias regulator.




A 144MHz design with the 6V2300

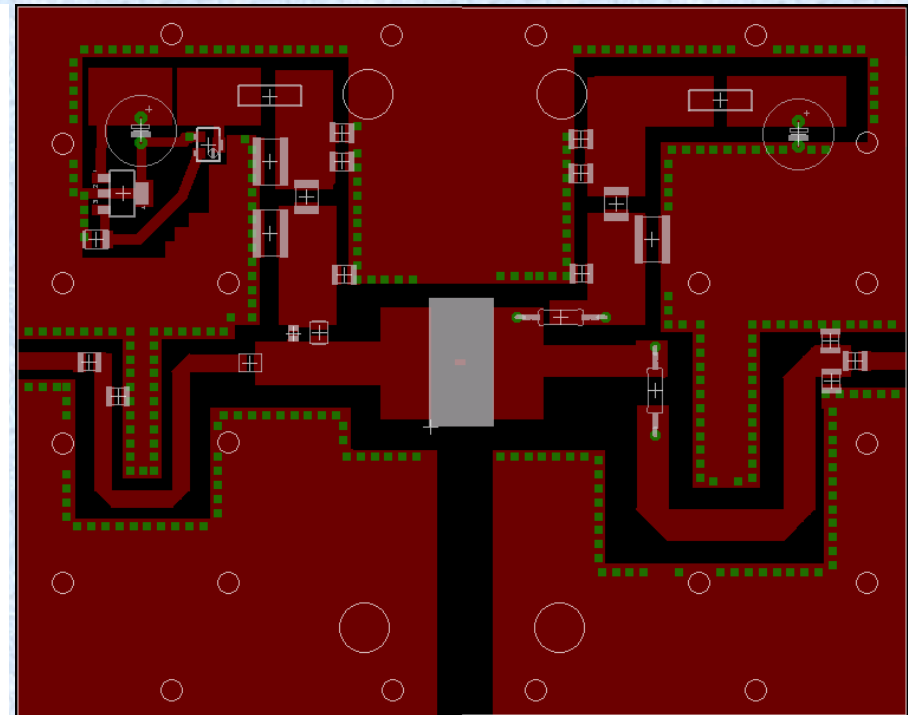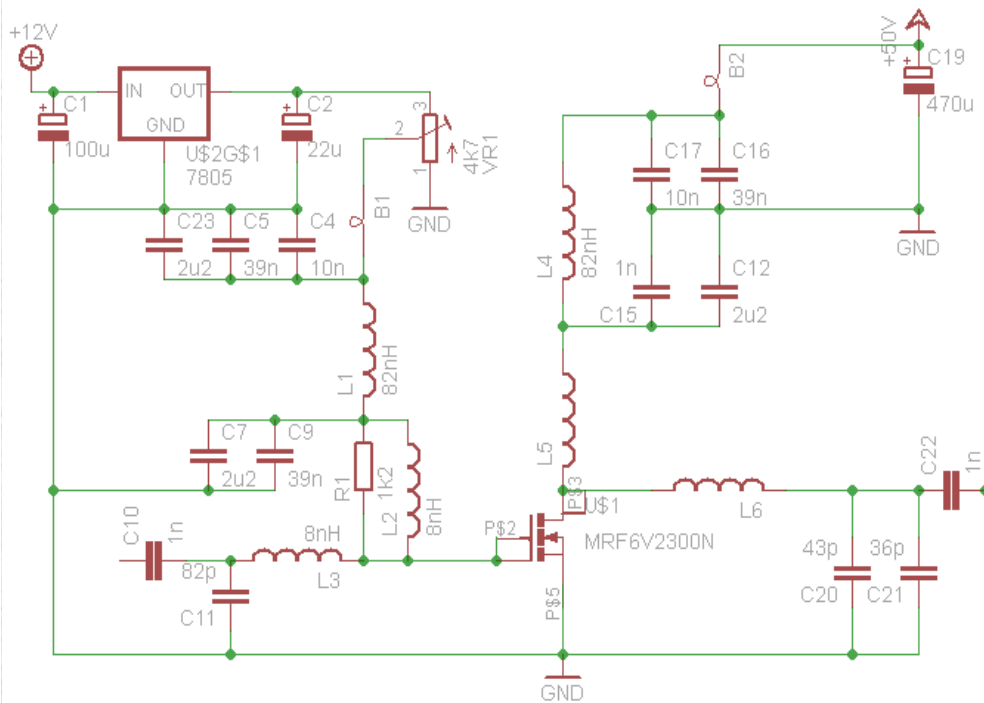- Eagle PC design done with bias regulator.



A wideband design with the MRF6V2600H

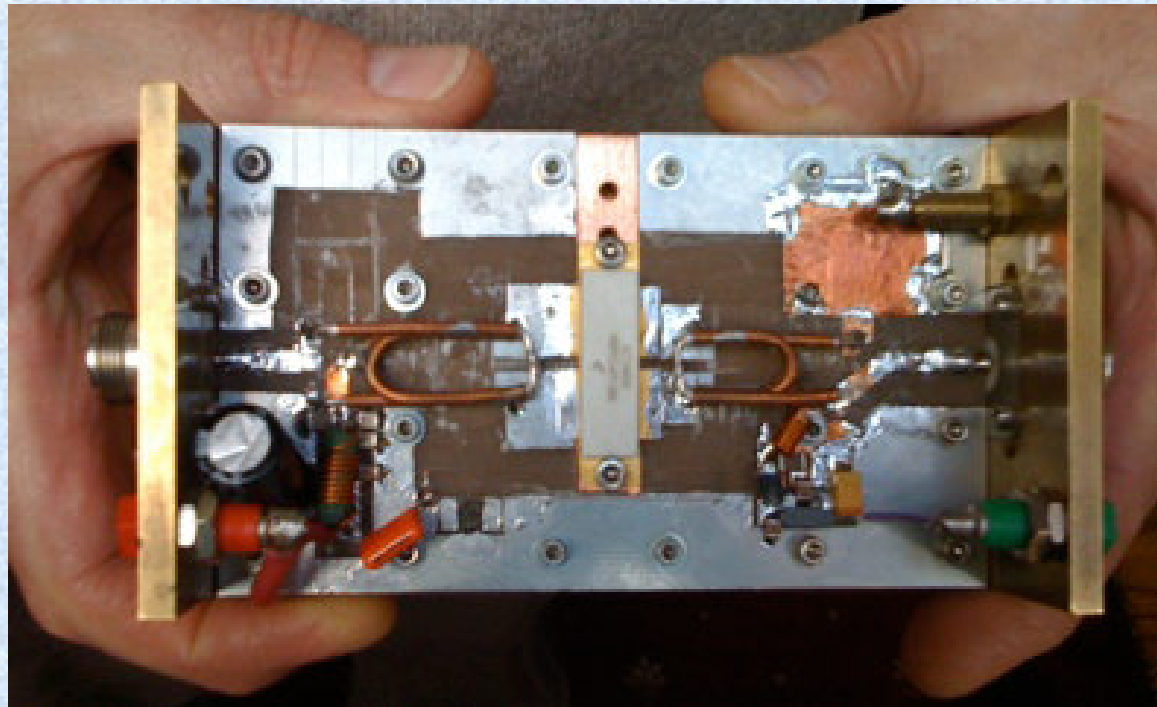- Target
 - 400W PEP 4m and 6m
- Flanged device
- Under development
 - Not powered up yet!
- Uses transformer matching



Do's and don'ts

- Get the heat away quickly!!
- DO Always use a copper heat spreader
- DO try and avoid shunt capacitors (losses)
- DO Watch the output capacitor's rating and type.
 - 100Watts in to 50 ohms means that 1.4 Amperes of RF is flowing.
- DON'T use trimmers except when "bodging".
 - Shunt capacitors have high currents as well
- DON'T put too much gate bias voltage!

Acknowledgements

- Freescale Applications Engineering (They Rock!)
- Bernie, G4HJW – “Bodger extraordinaire”
 - (And RF design professional :-)
- LDMOS pictures – ST Microelectronics
- “Smith” program Prof. Dellsperger Univ of Berne
- Appcad program